

Department of Electronics and Telecommunication Engineering

University of Moratuwa

B.Sc. (Eng) Semester 4
EN 2111-Electronic Circuit Design
Laboratory Experiment 01

Name: Chandrakumara H.A.D.C. Lab: Analog Lab
Index No: 230100M Group: 07
Date: 2026/01/28 Field: EN/BM

Marks:

First Order Filter Circuits

Objectives

To learn the frequency response of the first order active and passive filter circuits by experimental work.

Equipment

- Multimeter
- Function Generator
- Dual Power Supply
- Digital Oscilloscope (or CRO)
- Breadboard

Components

- OP-Amp (741)
- Resistors (180 Ω , 330 Ω , 1.5K Ω)
- Capacitors (0.1 μ F, 10nF)
- Wires

Theory

Filters alter the amplitude and/or phase characteristics of an electrical signal with respect to its frequency. A low-pass filter passes signals with a frequency lower than a cutoff frequency and attenuates signals with frequencies higher than the cutoff frequency. A high-pass filter passes signals with a frequency higher than a cutoff frequency and attenuates signals with frequencies lower than the cutoff frequency.

Types of Filters:

- Low pass Filter
- High pass Filter
- Band pass Filter
- Band stop Filter

Procedure

1.0 First Order Low-pass Filter Design

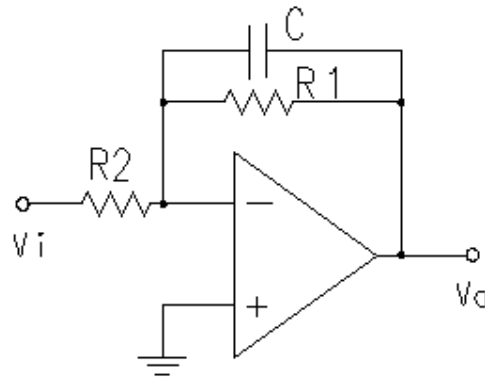



Figure 1: First Order Filter

- 1.1 Derive the transfer function of the circuit & determine the mid- band gain and the cutoff frequency. Identify the type of filter.
- 1.2 Calculate the values for R1, R2 and C to design a filter with 10 KHz cutoff frequency and a mid-band gain of 5. Select the components R1, R2, and C which are close to the calculated values.
- 1.3 Connect the circuit shown in Figure 1 with your selected components.
- 1.4 Connect a 200mV p-p sine wave to the input 'Vi' and change the frequency of the input signal as shown in Table 1. Measure the output voltage amplitude 'Vo p-p' and its phase shift introduced by the filter.

Frequency (KHz)	V _{o p-p}	Phase	Frequency (KHz)	V _{o p-p}	Phase
0.05	888mV	179 ⁰	8.0	696mV	133 ⁰
0.10	888mV	178 ⁰	10.0	632mV	130 ⁰
0.50	880mV	176 ⁰	15.0	472mV	122 ⁰
0.75	880mV	171 ⁰	20.0	408mV	119 ⁰
1.00	880mV	169 ⁰	30.0	344mV	112 ⁰
3.00	848mV	160 ⁰	50.0	332mV	97.2 ⁰
5.00	792mV	148 ⁰	100	286mV	88.4 ⁰

Table 1

1) 1.1).

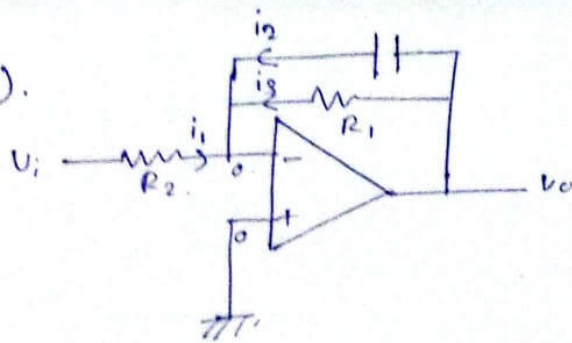

$$i_1(s) = \frac{V_i(s)}{R_2} \leftarrow (1) \quad i_2(s) = \frac{V_o(s)}{\left(\frac{1}{Cs}\right)}$$

$$i_3(s) = \frac{V_o(s)}{R_1} \leftarrow (2)$$

$$i_2(s) = Cs V_o(s) \leftarrow (3)$$

$$i_1(s) + i_2(s) + i_3(s) = 0$$

$$\frac{V_i(s)}{R_2} + Cs V_o(s) + \frac{V_o(s)}{R_1} = 0$$

$$V_o(s) \left(\frac{1 + CR_1 s}{R_1} \right) = -\frac{V_i(s)}{R_2}$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = -\frac{R_1}{R_2} \left(\frac{1}{1 + CR_1 s} \right)$$

$$H(j\omega) = -\frac{R_1}{R_2} \left(\frac{1}{1 + CR_1 j\omega} \right)$$

$$|H(j\omega)| = \frac{R_1}{R_2} \frac{1}{\sqrt{1 + (CR_1\omega)^2}} \Rightarrow \omega_c = \frac{1}{CR_1} \Rightarrow f_c = \frac{1}{2\pi R_1 C}$$

$$\text{mid-band gain} = -\frac{R_1}{R_2}$$


This is a low pass filter.

$$1.2) \frac{R_1}{R_2} = 5 \Rightarrow R_1 = 1.5 \text{ k}\Omega, R_2 = 330 \Omega$$

$$10 \text{ kHz} = \frac{1}{2\pi (1.5 \text{ k}\Omega) C} \Rightarrow C = 10.61 \text{ nF} \approx 10 \text{ nF}$$

$$\boxed{R_1 = 1.5 \text{ k}\Omega, R_2 = 330 \Omega, C = 10 \text{ nF}}$$


1.5 Plot the Gain vs Frequency.

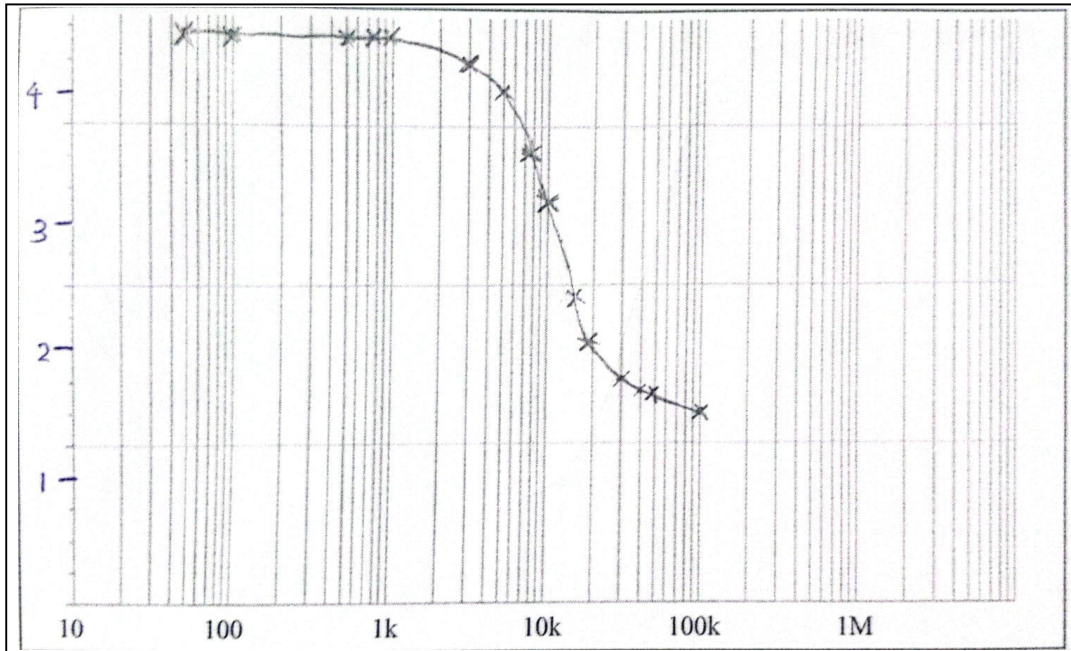

1.6 Connect a 100Ω ohm load to the output. Repeat the procedure given at section 1.4 and record the output ' V_o p-p' and its phase shift.

Frequency (KHz)	V_o p-p	Phase	Frequency (KHz)	V_o p-p	Phase
0.05	872mV	178°	8.0	668mV	128°
0.10	872mV	177°	10.0	580mV	120°
0.50	872mV	175°	15.0	440mV	118.8°
0.75	872mV	164°	20.0	352mV	108°
1.00	872mV	163°	30.0	232mV	100°
3.00	848mV	162°	50.0	158mV	95.4°
5.00	800mV	132°	100	120mV	88.5°

1.7 Plot the Gain vs Frequency.

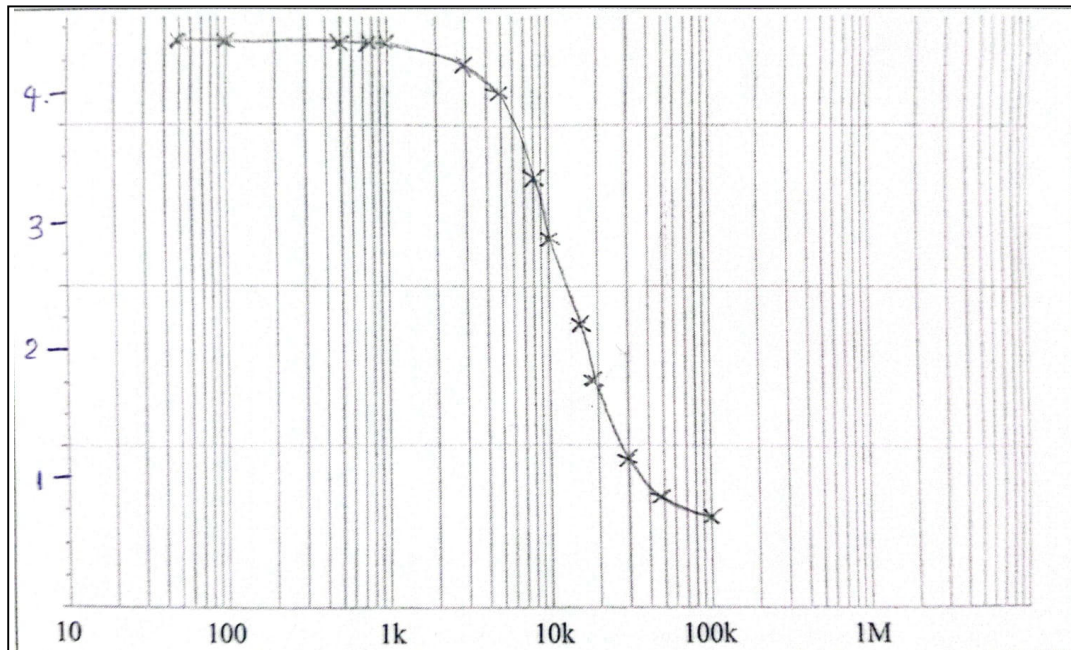

2.0 Connect the circuit shown in Figure 2 using the same components. Repeat the procedure given in Section 1.4.


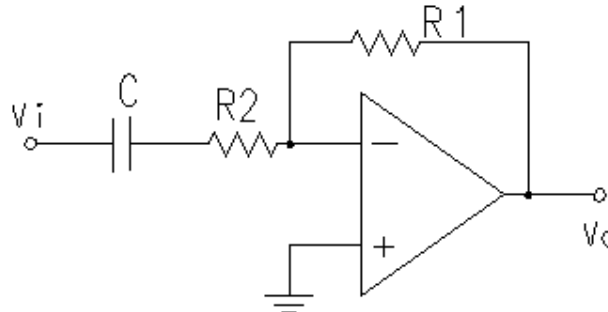


Figure 2

Frequency (KHz)	$V_{o\text{ p-p}}$	Phase	Frequency (KHz)	$V_{o\text{ p-p}}$	Phase
0.05	84mV	-	8.0	224mV	103.68°
0.10	86mV	115.2°	10.0	256mV	100.8°
0.50	90mV	107.99°	15.0	344mV	118.8°
0.75	99.2mV	97.19°	20.0	424mV	115.19°
1.00	114mV	100.8°	30.0	560mV	129.6°
3.00	120mV	97.19°	50.0	744mV	160.5°
5.00	160mV	100.8°	100	800mV	167.7°

2.1 Plot the Gain vs Frequency.

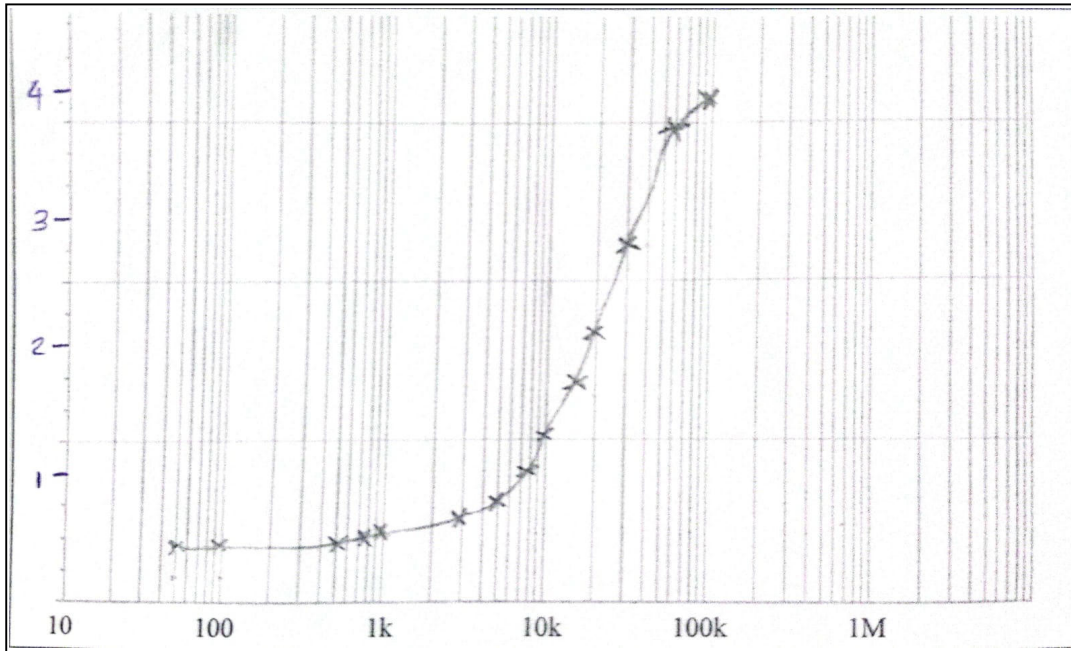

2.2 Discuss your observation and identify the type of filter.

- The gain of the filter increases with frequency, showing high attenuation at low frequencies while allowing high-frequency signals to pass with a gain approximately equal to 4.
- At low frequencies, the phase takes values close to 90° , and as the frequency increases, it approaches values close to 180° , resulting in an effective phase shift of 90° .

Therefore this is a high pass filter.